



ADHIYAMAAN COLLEGE OF ENGINEERING (AUTONOMOUS)

Department of Electrical & Electronics Engineering

A MINI PROJECT

on

POLICE SIREN LIGHT CIRCUIT USING IC555

Presented By

**G.ASHOK
S.DHANUSH
N.SATHISH**

**(6176AC22UEE005)
(6176AC22UEE011)
(6176AC22UEE055)**

Under the Supervision of
Dr. K. Santhi M.E., Ph.
D.
HOD & Professor / EEE.

Project Co-ordinator
Dr. K. Senthil M.E., Ph. D.
Professor / EEE.

CONTENTS

- **Introduction**
- **Objectives**
- **Existing methods**
- **Circuit diagram**
- **Hardware daigram**
- **List of components**
- **Conclusion**
- **Future scope**
- **References**

INTRODUCTION

- **We are going to make a Police Siren Circuit using two 555 timer IC. The circuit will produce an up-down wailing sound from the speaker. We will be using two 555 timer IC, so the circuit will be bit complex to make. We will fire first 555 is wired as a low frequency oscillator to control the voltage control pin 5 of the second 555. The voltage shift on pin 5 makes the frequency of the second oscillator to rise and fall. I will explain each step in detail with step wise execution and instructions of the circuit.**

OBJECTIVES


Generate Alternating Flashing Lights:

- **Use of 555 Timer IC:**
- **Frequency Control:**
- **Drive LEDs:**
- **Power Supply Considerations:**
- **Compact and Reliable Design:**
- **Safety and Heat Management:**

EXISTING METHODS


1. **IC 555 Timer:** The core component to generate the timing pulses.
2. **Resistors:** Typically, two resistors are used to set the timing intervals.
3. **Capacitor:** Used in conjunction with the resistors to determine the frequency of the oscillation.
4. **LEDs:** Usually two sets of LEDs to simulate the alternating flashing of a police siren.
5. **Transistors:** To amplify the current to drive multiple LEDs.
6. **Power Supply:** A suitable DC power source (e.g., 9V battery).

CIRCUIT DIAGRAM

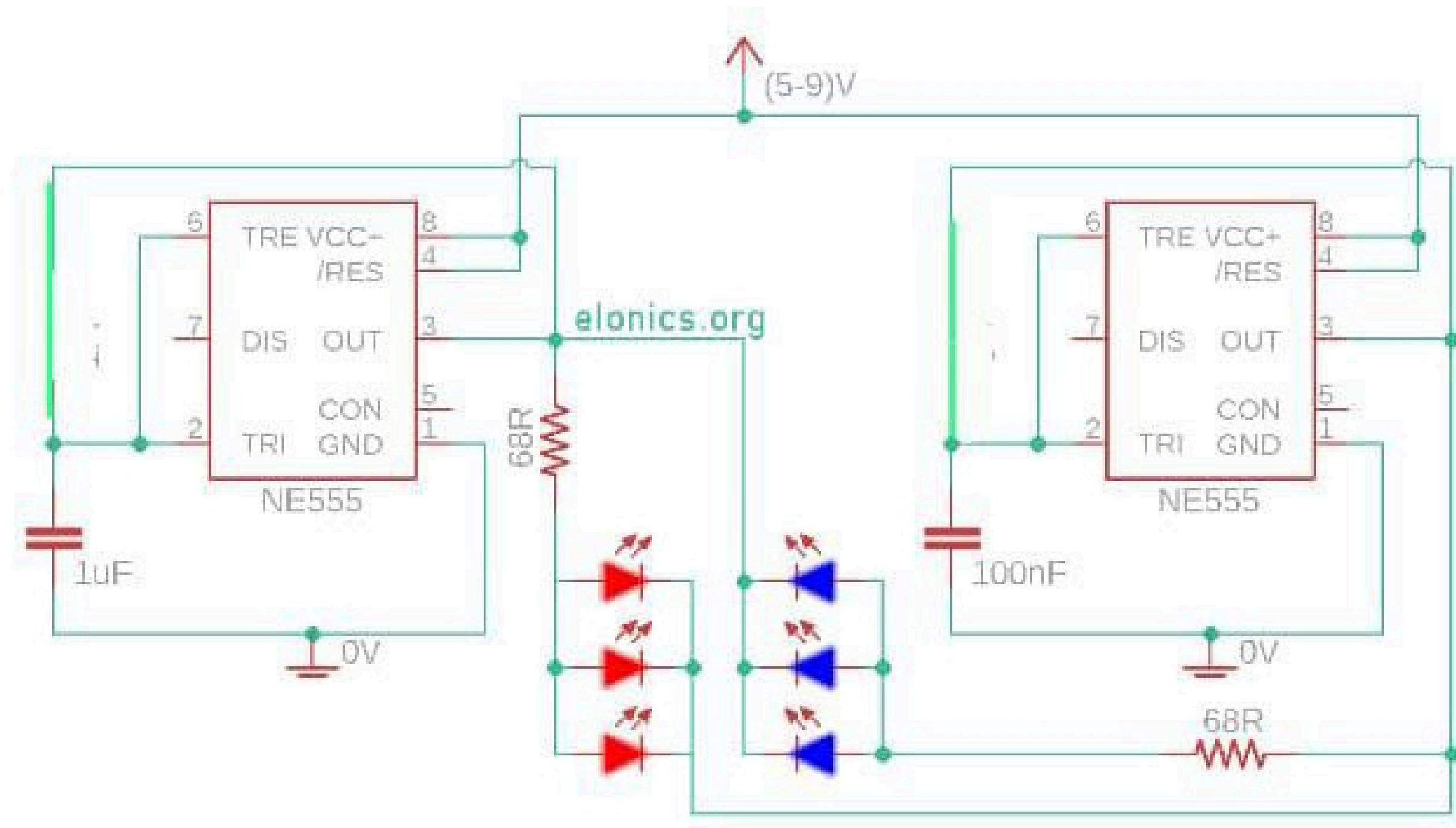

POLICE LIGHTS LED FLASHER CIRCUIT

HARDWARE DIAGRAM

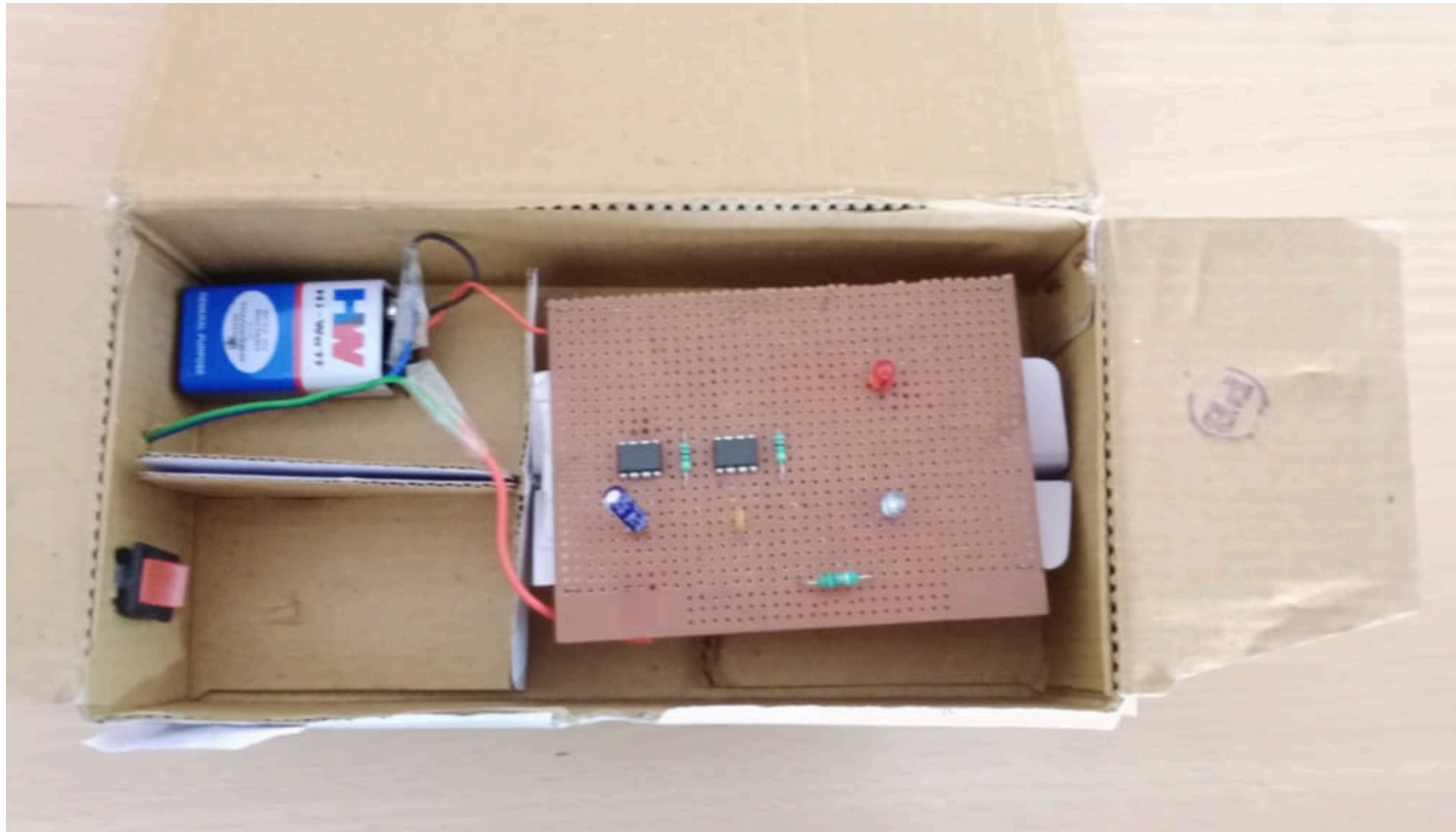

LIST OF COMPONENTS

- 1.IC 555 (2)
- 2.Resistors (1K-2)
- 3.Capacitors (2.2uF)
- 4.LEDs (red and blue for the police siren effect)
- 5.Power supply (typically 9V battery)
- 6.PCB board and connecting wires

CONCLUSION

- **The police siren light circuit using the IC 555 timer is a practical and straightforward project that demonstrates the versatility of the 555 timer IC. By configuring the 555 timer in astable mode, we were able to generate the necessary oscillations to drive the LED lights, simulating the flashing effect of a police siren. The project highlights several important concepts in electronics:**
 1. **Versatility of the 555 Timer:** The 555 timer IC proves to be an incredibly useful component for generating timing pulses. In this project, it was used to create an astable multivibrator, which produced the continuous square wave signals needed for the flashing lights.
 2. **Understanding Astable Mode:** Configuring the 555 timer in astable mode allows for the generation of a continuous output signal, which is essential for creating a repetitive flashing effect. This involves selecting appropriate resistor and capacitor values to achieve the desired frequency.
 3. **LED Driving Capability:** The circuit successfully demonstrated the ability to drive LEDs with the output from the 555 timer. By using transistors as switching elements, the circuit can handle higher current loads, enabling the operation of multiple LEDs simultaneously.
 4. **Practical Applications:** This project is not only a good educational tool but also has practical applications in various fields, such as emergency vehicle lighting, alarm systems, and decorative lighting.
 5. **Simplicity and Cost-Effectiveness:** The circuit is simple to build and requires minimal components, making it a cost-effective solution for creating flashing light effects.

FUTURE SCOPE

- **Integration with Modern Technologies:**
- **Microcontrollers and IoT:**
- **Wireless Control**
- **Enhanced Features**
- **Programmable Patterns**
- **Sound Modulation**
- **Energy Efficiency**
- **Low-Power Components**
- **Battery Management Systems**
- **Safety and Compliance**

REFERENCES

- **Datasheet of 555 Timer IC:**
- Provides detailed information on the functionality, pin configuration, and applications of the 555 timer IC.
- NE555 Datasheet
- **Basic 555 Timer Circuits:**
- Various examples of 555 timer circuits including astable and monostable multivibrators.
- 555 Timer Circuits
- **Police Siren Circuit Examples:**
- Example circuits using 555 timer IC to create police siren effects.
- Police Siren Circuit
- Flashing Police Lights

THANK YOU!